

# Hierophone Filter

Guy John  
guy@rumblesan.com

July 14, 2025

## 1 Introduction

Analysis of the Hierophone filter, a basic three-pole low-pass filter built from three cascaded OTA based integrator cells.

## 1.1 Notations

$R_i$  is the value of the resistor through which the input signal is fed to the OTA

$R_s$  is the value of the resistor at the voltage divider input of the OTA

$R_f$  is the value of the resistor through which the integrator output is fed back to the OTA input


$C$  is the value of the integrators' capacitor

$v_{cv}$  is the cutoff frequency control voltage

$v_i(s)$  is the input voltage

$v_{out}(s)$  is the output voltage

## 1.2 OTA Low-Pass Filter

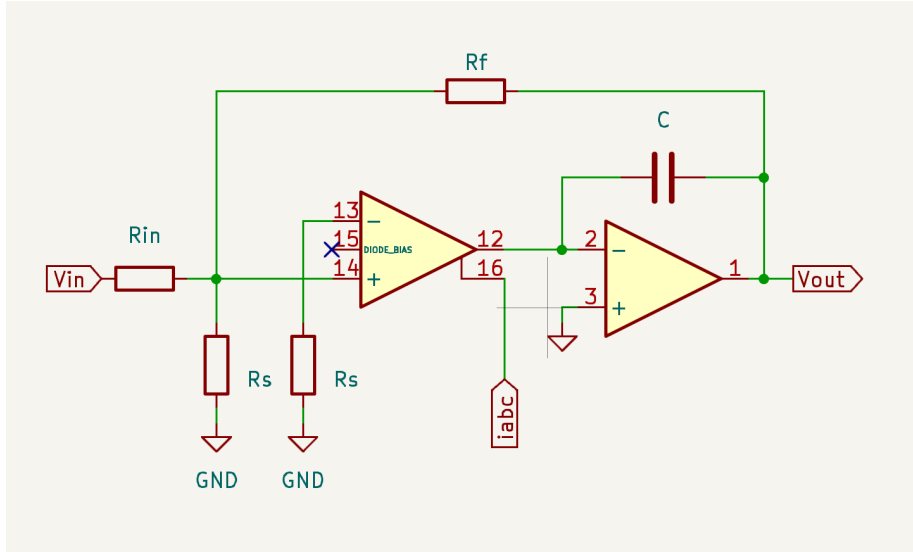

The transfer function of an OTA is:

$$i_o = g_m(v_+ - v_-)$$

$$i_o = 19.2i_{cv}(v_+ - v_-)$$

If  $R_f = R_i = R$  then Kirchoff in  $v_+$  gives:

$$\frac{1}{R}(v_i(s) - v_+(s)) + \frac{1}{R}(v_{out}(s) - v_+(s)) = \frac{1}{R_s}v_+(s)$$

$$v_+(s) = \frac{R_s}{R + 2R_s}(v_i(s) + v_{out}(s))$$

Given that  $v_-$  is grounded, the current  $i_c(s)$  at the output of the OTA is:

$$\begin{aligned} i_c(s) &= g_m(v_+(s) - v_-(s)) \\ &= 19.2i_{cv} \frac{R_s}{R + 2R_s} (v_i(s) + v_{out}(s)) \end{aligned}$$

The voltage out of the OpAmp:

$$\begin{aligned} v_{out}(s) &= \frac{-i_c(s)}{C_s} \\ v_{out}(s) &= -19.2i_{cv} \frac{R_s}{C_s(R + 2R_s)} (v_i(s) + v_{out}(s)) \end{aligned}$$

So the transfer function is:


$$\alpha(s) = \frac{-1}{1 + \frac{R + 2R_s}{R_s} C_s \frac{1}{19.2i_{cv}}} \quad (1)$$

The pole is at the frequency  $f$  so that:

$$\begin{aligned} 0 &= 1 + \frac{R + 2R_s}{R_s} C_s 2\pi f \frac{1}{19.2i_{cv}} \\ f &= -\frac{19.2i_{cv}}{2\pi \frac{R + 2R_s}{R_s} C} \end{aligned}$$

### 1.3 Feedback Control

The gain of the feedback circuit is:

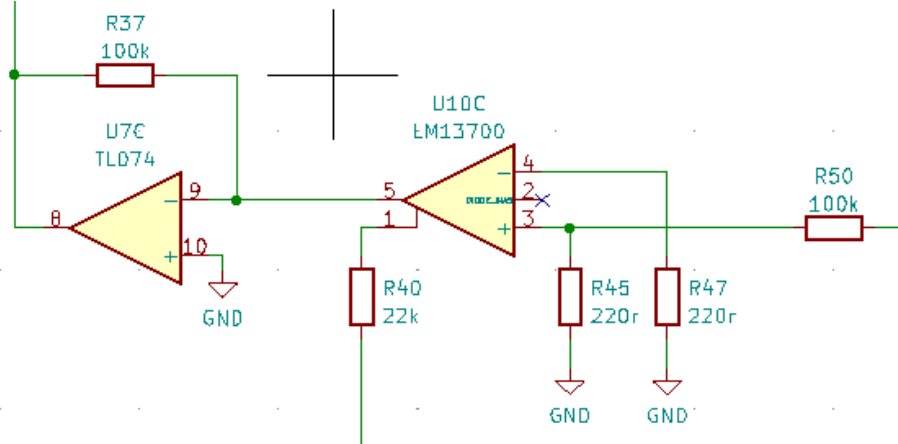

$$\begin{aligned}
v_+ &= v_i \frac{R_s}{R + R_s} \\
i_o &= 19.2i_q(v_+ - v_-) \\
i_o &= 19.2i_q(v_+ - 0) \\
i_o &= 19.2i_q v_i \frac{R_s}{R + R_s} \\
i_o &= R_f(v_- - v_o) \\
i_o &= -R_f v_o \\
-R_f v_o &= 19.2i_q v_i \frac{R_s}{R + R_s} \\
-R_f v_o &= 19.2i_q v_i \frac{R_s}{R + R_s} \\
v_o &= -19.2i_q v_i \frac{R_f R_s}{R_i + R_s} \\
\beta &= -19.2i_q \frac{R_f R_s}{R_i + R_s}
\end{aligned}$$

#### 1.4 Filter

$$\begin{aligned}
\frac{v_i - v_-}{R_i} + \frac{v_{hp} - v_-}{R_g} + \frac{v_{lp} - v_-}{R_g} + \frac{v_{bp}\beta - v_-}{R_q} &= i_- = 0 \\
\frac{v_i}{R_i} + \frac{v_{hp}}{R_g} + \frac{v_{lp}}{R_g} + \frac{v_{bp}\beta}{R_q} &= 0
\end{aligned}$$

It is important to note that  $v_{bp}(s) = v_{hp}(s)\alpha(s)$ , and  $v_{lp}(s) = v_{hp}(s)\alpha(s^2)$ .

#### 1.4.1 High-pass

$$\begin{aligned}
\frac{v_{hp}(s)}{R_g} &= -\frac{v_i(s)}{R_i} - \frac{v_{lp}(s)}{R_g} - \frac{v_{bp}(s)\beta}{R_q} \\
\frac{v_{hp}(s)}{R_g} &= -\frac{v_i(s)}{R_i} - \frac{v_{hp}(s)\alpha(s^2)}{R_g} - \frac{v_{hp}(s)\alpha(s)\beta}{R_q} \\
\frac{v_i(s)}{R_i} &= -\frac{v_{hp}(s)}{R_g} - \frac{v_{hp}(s)\alpha(s^2)}{R_g} - \frac{v_{hp}(s)\alpha(s)\beta}{R_q} \\
H_{hp}(s) &= \frac{v_{hp}(s)}{v_i(s)} \\
\frac{v_i(s)}{R_i} &= -v_{hp}(s)\left(\frac{1}{R_g} + \frac{\alpha(s^2)}{R_g} + \frac{\alpha(s)\beta}{R_q}\right) \\
\frac{1}{R_i} &= -H_{hp}(s)\left(\frac{1}{R_g} + \frac{\alpha(s^2)}{R_g} + \frac{\alpha(s)\beta}{R_q}\right) \\
\frac{-1}{R_i} &= H_{hp}(s)\left(\frac{1}{R_g} + \frac{\alpha(s^2)}{R_g} + \frac{\alpha(s)\beta}{R_q}\right) \\
H_{hp}(s) &= \frac{-1/R_i}{\frac{1}{R_g} + \frac{\alpha(s^2)}{R_g} + \frac{\alpha(s)\beta}{R_q}} \\
&= \frac{-R_g/R_i}{1 + \frac{R_g\alpha(s)\beta}{R_q} + \alpha(s^2)}
\end{aligned}$$

### 1.4.2 Low-Pass

$$\begin{aligned}
H_{lp}(s) &= \frac{v_{lp}(s)}{v_i(s)} \\
&= \frac{v_{hp}(s)}{v_i(s)} \alpha^2(s) \\
&= \frac{-R_g/R_i}{\frac{1}{\alpha^2(s)} + \frac{R_g\beta}{R_q\alpha(s)} + 1} \\
&= \frac{-R_g/R_i}{\frac{1}{\alpha^2(s)} + \beta \frac{R_g}{R_q} \frac{1}{\alpha(s)} + 1} \\
&= \frac{-R_g/R_i}{\frac{1}{(-19.2i_{cv} \frac{R_s}{Cs(R+2R_s)})^2} + (-19.2i_q \frac{R_f R_s}{R_i + R_s}) \frac{R_g}{R_q} \frac{1}{-19.2i_{cv} \frac{R_s}{Cs(R+2R_s)}} + 1} \\
&= \frac{-R_g/R_i}{\frac{1}{(19.2i_{cv} \frac{R_s}{Cs(R+2R_s)})^2} + 19.2i_q \frac{R_f R_s}{R_i + R_s} \frac{R_g}{R_q} \frac{1}{19.2i_{cv} \frac{R_s}{Cs(R+2R_s)}} + 1} \\
&= \frac{-R_g/R_i}{\frac{1}{\frac{1}{s^2} (19.2i_{cv} \frac{R_s}{Cs(R+2R_s)})^2} + 19.2i_q \frac{R_f R_s}{R_i + R_s} \frac{R_g}{R_q} \frac{1}{19.2i_{cv} \frac{1}{s} \frac{R_s}{Cs(R+2R_s)}} + 1} \\
&= \frac{-R_g/R_i}{\frac{s^2}{(19.2i_{cv} \frac{R_s}{Cs(R+2R_s)})^2} + 19.2i_q \frac{R_f R_s}{R_i + R_s} \frac{R_g}{R_q} \frac{s}{19.2i_{cv} \frac{R_s}{Cs(R+2R_s)}} + 1}
\end{aligned}$$

One simplification worth making is to say that  $R_q = R_g$ .

By comparing with the standard form of a second order filter transfer function we can work out the following.

Pass-band gain,  $-\frac{R_g}{R_i}$

Cutoff frequency,  $19.2i_{cv} \frac{R_s}{C2\pi(R+2R_s)}$

Quality factor,  $\frac{1}{19.2i_q \frac{R_f R_s}{R_i + R_s}}$

### 1.5 Calculating cutoff frequencies

Given the calculation for frequency, and picking some standard values we can calculate cutoff for different  $i_{cv}$  values.

$R$  is 100k

$R_s$  is 220r

$C$  is 220pF

$$f = 19.2i_{cv} \frac{220}{220 * 10^{-12} * 2\pi(100000 + 2(220))} \quad (2)$$

for  $i_{cv}$  of 0.5ma  $f = 15212Hz$

for  $i_{cv}$  of 0.3ma  $f = 9127Hz$

for  $i_{cv}$  of 0.1ma  $f = 3042Hz$

for  $i_{cv}$  of 0.05ma  $f = 1521Hz$

for  $i_{cv}$  of 0.01ma  $f = 304Hz$

## 1.6 Calculating resonance

A quality factor of 1/2 gives no resonance, whilst the resonance (and likelihood of self oscillating) increases as Q goes to infinity.

$R_f$  is 100k

$R_i$  is 100k

$R_s$  is 220r

$C$  is 220pF

$$q = \frac{1}{19.2i_q \frac{100000*220}{100000+220}} \quad (3)$$

for  $i_q$  of 0.5ma  $q = 0.47$

for  $i_q$  of 0.3ma  $q = 0.79$

for  $i_q$  of 0.1ma  $q = 2.37$

for  $i_q$  of 0.05ma  $q = 4.75$

for  $i_q$  of 0.01ma  $q = 23.7$